



NGSPICE - XSPICE ELEMENTAL DEVICES MADE AVAILABLE IN KiCAD

Holger Vogt

Duisburg, Germany | 01.02.2025



Offen im Denken


Contents

- Intro to the ngspice circuit simulator
- What is new in ngspice ?
- XSPICE code models in ngspice
- KiCad supporting code models
- Simulation examples
- What is next in ngspice ?

ngspice – what is it ?

Circuit simulator that numerically solves equations describing (electronic) circuits made of passive and active devices for (time varying) currents and voltages.

 Open source successor of venerable spice3f5 from Berkeley



```
CMOS inverter

.include ./bsim4soi/nmos4p0.mod
.include ./bsim4soi/pmos4p0.mod
.option TEMP=27C

Vpower VD 0 1.5
Vgnd VS 0 0


Vgate Ein VS PULSE(0 1.5 100p 50p 50p 200p 500p)

MN0 Aus Ein VS VS N1 W=10u L=0.18u
MP0 Aus Ein VD VS P1 W=20u L=0.18u

.tran 3p 600ps

.control
  run
  plot Ein Aus
.endc

.END
```

 


the circuit


the input

the output

KiCad/ngspice Interface

 

KiCad/Eeschema simulator window

 

What's new in ngspice?

- Current release ngspice-44.2 from Jan. 11th, 2025
- Support for Verilog-A compact device models and analog building blocks
- Co-simulation ngspice mixed-signal – Verilog digital (using Verilator, or Icarus Verilog)
- Co-simulation ngspice mixed-signal – VHDL digital (using GHDL) *
- Co-simulation ngspice mixed-signal – C-coded digital
- Degradation simulation (stress, radiation)

<https://sourceforge.net/projects/ngspice/files/ng-spice-rework/44.2/> <https://ngspice.sourceforge.io/>

* <https://sourceforge.net/p/ngspice/ngspice/ci/pre-master-45/tree/> (development branch)

ngspice and Verilog-A co-simulation

```
// importing libs
`include "discipline.h"

module diff_amp(
    output electrical out,
    input electrical in1,
    input electrical in2);

parameter real gain = 40; // setting gain to 40 of the differential amplifier
parameter real vcc = 3; // swing from -vcc to +vcc
parameter real offset = 3; // added offset

analog begin
    V(out) <+ offset / 2 + vcc / 2 * tanh( gain / vcc * 2 * V(in1, in2));
end
endmodule
```

Compile with OpenVAF



Model in shared library

```
.subckt diff_amp_cell OUT IN1 IN2
N1 out in1 in2 diff_amp_model
.ends diff_amp_cell

.model diff_amp_model diff_amp
```

Call to model in the ngspice netlist

Verilog-A model of a simple differential amplifier


Ngspice and Verilog-A cosimulation with Xschem

Author Stefan Schippers

https://www.youtube.com/watch?v=g9WPjZ_e8co

ngspice and Verilog-A

```
create a diff_amp.v file with following code  
and compile it into a .osdb file with openvaf.  
  
// importing libs  
'include "discipline.b"  
  
module diff_amp(  
    .output electrical out,  
    .input electrical in1,  
    .input electrical in2);  
  
parameter real gain = 40; // setting gain to 40 of the differential amplifier  
parameter real vcc = 3.3; // swing from -vcc to +vcc  
parameter real offset = 3; // added offset  
  
analog begin  
    V(out) == offset / 2 + vcc / 2 * tanh(gain * vcc * 2 * V(in1, in2));  
end  
endmodule
```

 


COMMANDS

```
:options savecurrents  
:control  
    save all  
    op  
    remzerovec  
    write tb_diff_amp.raw  
    dc V1 1.1 1.9 0.001  
    set appendwrite  
    remzerovec  
    write tb_diff_amp.raw  
    quit 0  
endc
```

→ OP annotate

→ load waves

Opamp gain

 


V(v-sweep)

b

a

z

 


V(v-sweep)


ngspice and Verilog/VHDL mixed-signal co-simulation

ngspice analog and
Verilator/Iverilog/
GHDL event based
co-simulation

 
(but also
Ngspice analog and
internal XSPICE
event based
co-simulation)



 ngspice and Verilog mixed-signal co-simulation



DAC output:
Summed-up
current

 

Analog module:
DAC with weighted current
mirrors and switches

Digital module:
Counter

Compile with
Verilator
Link to ngspice

```
module dig(
    input wire clk,
    input wire reset,
    output logic [4:0] b
);

logic rst = 0;

always_ff @ (posedge clk) begin
    if(reset)
        rst <= 1;
    else
        rst <= 0;
end

always_ff @ (posedge clk) begin
    if(rst)
        b <= 0;
    else
        b <= b + 1;
end // dig
endmodule
```

ngspice and Verilog mixed-signal co-simulation

Mixed Signal Simulation in Ngspice

Author: Carsten Wulff

<https://www.youtube.com/watch?v=vEZPCIInwmQ&t=1689s>

<https://analogicus.com/aic2025/2024/12/06/Mixed-Signal-Simulation-in-NGSPICE.html>


Tutorial at http://analogicus.com/jnw_sv_sky130a/

Repository at https://github.com/wulffern/jnw_sv_sky130a

Assumes knowledge of <https://analogicus.com/aic2025/2025/01/01/Sky130nm-tutorial.html>

Interface to ngspice: d_cosim code model: Giles Atkinson

 ngspice and C code mixed-signal co-simulation




Author: Stephen, @slh

<https://forum.kicad.info/t/easier-mixed-mode-simulation-and-real-world-comparison/56530>


<https://forum.kicad.info/t/mixed-mode-simulation-including-c-code-and-verilog/49752>

Interface to ngspice: d_process code model: Uros Platise, Brian Taylor

 ngspice and C code mixed-signal co-simulation





DC-DC-converter Simulation

 


Measurement

  Simulation of a CMOS Circuit after Hot Carrier Degradation




Green: before voltage stress
Red: after voltage stress

 Hot Carrier Degradation of a MOS transistor




Ring Oscillator

 

XSPICE in ngspice

- Conceived by Georgia Tech in 1990/91 as an extension of Spice3f.
- Fully integrated into ngspice since its beginning.
- Enables co-simulation of analog blocks and digital event based blocks.
- More than 60 blocks (named ‘code models’) are provided with the ngspice distribution.
- Digital simulation is fast, but lacks waveform details.
- User may create his/her own code models (C code with predefined macros).


ngspice/XSPICE Top-Level Diagram

 

Why XSPICE/ngspice support in KiCad?

- Task: create and simulate electronic systems.
- Use KiCad/Eeschema/ngspice simulation capability.
- Facilitate the use of the code models.
- Schematic entry at block level.
- Building blocks for system evaluation, not linked to PCB design.
- May be combined with the Verilog-A and HDL digital approaches described before.


XSPICE Elemental Devices

 


How to install the code models in KiCad?

- Download XSPICE-symbols-models-4.7z from
<https://forum.kicad.info/t/simulation-with-xspice-code-models/56384/3> .
- Expand and save both files into the KiCad symbol directory (C:\Program Files\KiCad\8.0\share\kicad\symbols on MS Windows). Simulation_XSPICE.kicad_sym contains the symbols, Simulation_XSPICE.sp the associated ngspice models.
- Add the symbols to the list of available symbols via the KiCad Symbol Editor.

Example: Amplitude Modulation

 

2.5 kW class D audio amplifier

 

Example: Audio Driver

```
* Class D audio amp frontend (to drive a power MOS half bridge)
* analog input
* pwm clock generator
* digital one-shot
* non-overlapping clock
* two floating half-bridge drivers
```

Started with netlist, difficult to read after some time

```
* Calling the subcircuit
* Xpwm ain lo+ lo- hi+ hi- DAudioDriver freq = 500k dtime = 100n voutp = 1.4 voutn = 0
```

```
.subckt DAudioDriver ain lo+ lo- hi+ hi- params: freq = 317k dtime = 50n voutp = 12 voutn = 0
```

```
apwm1 ain dfast1 pwm_osc
```

```
.model pwm_osc d_pwm(cntl_array = [-2 -1.99 1.99 2]
```

```
+ dc_array = [0.1 0.1 0.9 0.9]
```

```
+ frequency = {freq} init_phase = 90.0
```

```
a6 dfast1_d1 inv1
```

```
.model inv1 d_inverter(rise_delay = 0.3e-9 fall_delay = 0.3e-9
+ input_load = 0.5e-12)
```

```
* equalize d1 and _d1
```

```
abuf2 dfast1 d1 buf2
```

```
.model buf2 d_buffer(rise_delay = 0.3e-9 fall_delay = 0.3e-9
+ input_load = 0.5e-12)
```

```
*** one-shot ***
* buffer
```

```
abuf1 dfast1 d2 buf1
.model buf1 d_buffer(rise_delay = {dtime} fall_delay = {dtime}
+ input_load = 0.5e-12)
* one-shot 1->0 output
```

```
a9 [dfast1 d2] dos xnor3
```

```
.model xnor3 d_xnor(rise_delay = 0.2e-9 fall_delay = 0.2e-9
+ input_load = 0.5e-12)
***
```

```
* outputs: inverted, non-overlapping
```

```
aand1 [dout1 dos] dout1 and1
```

```
aand2 [_d1 dos] dout2 and1
```

```
.model and1 d_and(rise_delay = 0.4e-9 fall_delay = 0.4e-9
+ input_load = 0.5e-12)
```

```
* analog out, differential
```

```
abridge1 [dout1] %vd(lo+ lo-) dac1
```

```
abridge2 [dout2] %vd(hi+ hi-) dac1
```

```
.model dac1 dac_bridge(out_low = {voutn} out_high = {voutp} out_UNDEF = 0
+ input_load = 5.0e-12 t_rise = 20e-9
+ t_fall = 20e-9)
```

```
* test
```


```
* do we have overlap?
```

```
* aandtest [dout1 dout2] dtest and1
```

```
.ends
```

Much better to read, create netlist by exporting

 
```
.param dtime=100n freq=317k olo=0 ohi=12
```



* measure simulation time:
.control
set controls wait
rusage time
.endc

 Example: Audio Driver

Simulation of the half bridge power transistor driver over one input period



Example: Lorenz Attractor


$$\frac{dx}{dt} = 10(y - x)$$

$$\frac{dy}{dt} = 28x - y - xz$$


$$\frac{dz}{dt} = xy - \frac{8z}{3}$$

Author: cbias
<https://forum.kicad.info/t/x-y-plot-lorenz-attractor-using-a-models/56382>
 
```
.control
set controlswait
set nolegend
gnuplot D:\gnuplot Z vs X title 'Lorenz Attractor' xlabel 'X' ylabel 'Z'
.endc
```



Example: Lorenz Attractor

 

Independently developed by cblas,
using his own symbols with the
ngspice code models

An analog computer, solving three
dependent differential equations,
simulated on a digital machine.

Uses gnuplot for the X-Z plot

What's next in ngspice?

Some ideas, some more or less fixed plans, some actual activities:

- Improve RF capability by adding Harmonic Balance **ongoing**
- Support for reliability and degradation simulation **ongoing**
- Simulation of transient noise
- Improve usability of KiCad/ngspice graphics interface **ongoing**
- Support for ngspice mixed signal building blocks in Eeschema **ongoing**
- Enhance compatibility with LTSPICE models (A devices?)
- Test and improve the Verilog/VHDL/C interfaces
- Use AI for faster model building and simulation

Current development branch at git: <https://sourceforge.net/p/ngspice/ngspice/ci/pre-master-45/tree/>

Support

Ngspice discussion forums <https://sourceforge.net/p/ngspice/discussion/>

Ngspice Manual <https://ngspice.sourceforge.io/docs.html>

KiCad-Info forum <https://forum.kicad.info/>

KiCad Manual (V8) <https://docs.kicad.org/8.0/en/eeschema/eeschema.html#simulator>

Tutorials <https://ngspice.sourceforge.io/tutorials.html>

Models, model parameters <https://ngspice.sourceforge.io/modelparams.html>

Simulation examples

<https://sourceforge.net/p/ngspice/ngspice/ci/master/tree/examples/>

<https://forum.kicad.info/t/simulation-examples-for-kicad-eeschema-ngspice/34443>

<https://forum.kicad.info/t/more-simulation-examples-for-kicad-eeschema-ngspice/45546>

<https://forum.kicad.info/t/simulation-with-xspice-code-models/56384/2>